

Assignment

Name: Bilal Haneef

Roll #: 44

Teacher: Miss Maleeha Anwar

Topic: Multiplexer and De- Multiplexer

Section: Sec A (Evening)

Difference between Multiplexer and De- Multiplexer

Multiplexer	De-Multiplexer
Multiplexer is a combinational circuit that has maximum of 2^n data inputs, 'n' selection lines and single output line. One of these data inputs will be connected to the output based on the values of selection lines.	De-Multiplexer is a combinational circuit that performs the reverse operation of Multiplexer. It has single input, 'n' selection lines and maximum of 2^n outputs. The input will be connected to one of these outputs based on the values of selection lines.
Multiplexer takes two or a lot of signals and returns single output.	De-multiplexer reverses what the multiplexer does.
Communication system use multiplexer to carry multiple data like audio, video and other form of data using a single line for transmission.	The demultiplexer receive the output signals of the multiplexer and converts them back to the original form of the data at the receiving end.
A multiplexer is used in telephone networks to integrate the multiple audio signals on a single line of transmission.	In an ALU circuit, the output of ALU can be stored in multiple registers or storage units with the help of demultiplexer .

Multiplexer of 8x1:

Multiplexer of 8x1 has 8 input lines and 1 output lines,

Select lines will be , $2^s = n$, $2^s = 8$, $2^s = 2^3$, $s = 3$

Truth Table:

S ₀	S ₁	S ₂	Output
0	0	0	O ₀
0	0	1	O ₁
0	1	0	O ₂
0	1	1	O ₃
1	0	0	O ₄
1	0	1	O ₅
1	1	0	O ₆
1	1	1	O ₇

Circuit Diagram:

